




THE NUMBER ONE DODGE/CUMMINS TURBO DIESEL RESOURCE

# ISSUE 65 AUG/SEPT/OCT 2009



ENTER THE 2010 TDR CALENDAR COMPETITION! DETAILS ON PAGE 8.

# MEMBER 2 MEMBER

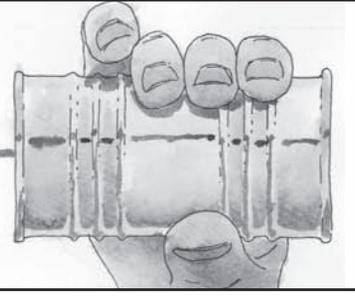

*I think you will agree with me when I categorize Turbo Diesel owners as independent people who are not afraid to try something new. You are an ingenious membership who reinvents and improves a product to make it better serve your needs. You show a strong willingness to share your shadetree solutions. With your input each quarter, we publish the "Member2Member" exchange to give you a forum to tell other members how you solved a problem.*

## THEORY AND APPLICATION OF THE AUTOMOTIVE RELAY

by Ryan Battelle

In this article we'll explore, in simple terms, what relays are, and why you should be using them in your wiring projects.

### What is a relay?

A relay is a switch. It's as simple as that. Just like the switches in your house, or your headlight switch, a relay is meant to do exactly one thing: control the flow of electricity. And just like a switch, relays are either "on" or "off" at any given moment.

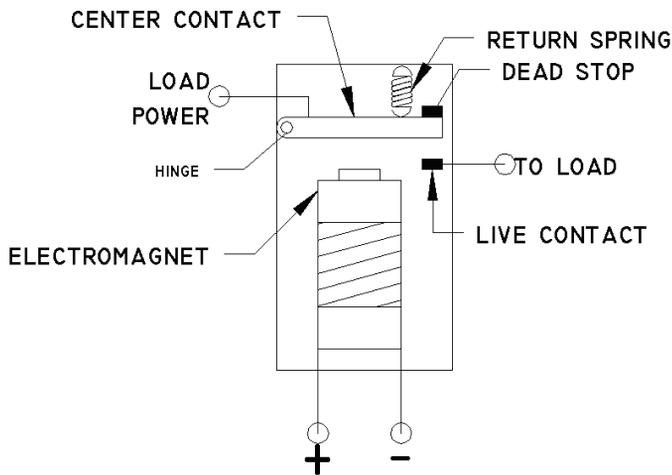


Figure 1: a single-pole, single-throw relay (SPST).

Relays have two fundamental parts: an electromagnet and a set of contacts (see figure 1). As the name implies, an electromagnet produces a magnetic field when a current passes through a wire coiled around a piece of iron. The center contact (as labeled) is made of steel and hinged at one end. When a current is applied to the + and - terminals in figure 1, a magnetic field forms, which draws the center contact down to the live contact.

The center contact is connected to a power source (labeled "Load Power" in figure 1). Since the center contact is conductive, when it is applied to the live contact, power flows through the center contact and out to whatever you've got connected to the live contact.

When current is removed from the + and - terminals, magnetism dissipates, and the center contact is drawn back up to the dead stop by the return spring.

Figure 1 depicts a single-pole, single-throw relay (commonly specified as SPST). That means it has exactly one center contact, and exactly one live contact. SPST relays are used, obviously, to switch a circuit on or off, just like a toggle switch.

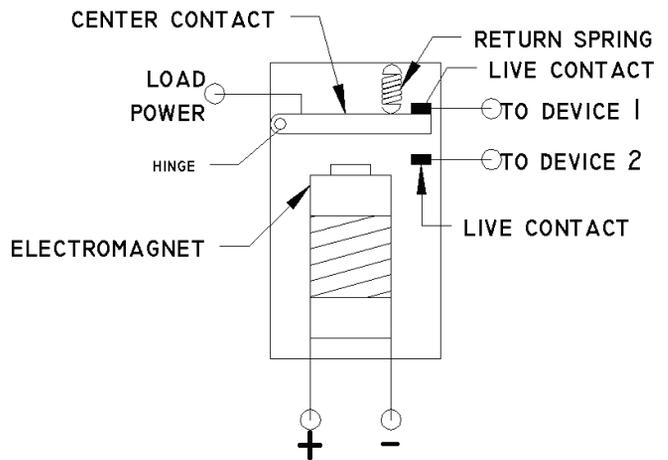


Figure 2: a single-pole, double-throw relay (SPDT).

Figure 2 depicts a single-pole, double-throw relay (SPDT). As shown, such a relay has a single center contact like an SPST, but two live contacts. The upper contact in the figure is live when the electromagnet is off, whereas the lower contact is live when the electromagnet is on. These are useful in applications where you need two different devices to be activated depending on the position of a single switch. For example, let's say you wanted to be able to monitor both front and rear axle fluid temperature from a single gauge in the cab. You could wire each temperature sensor to its own live contact in figure 2, and then use a toggle switch to select between the two.

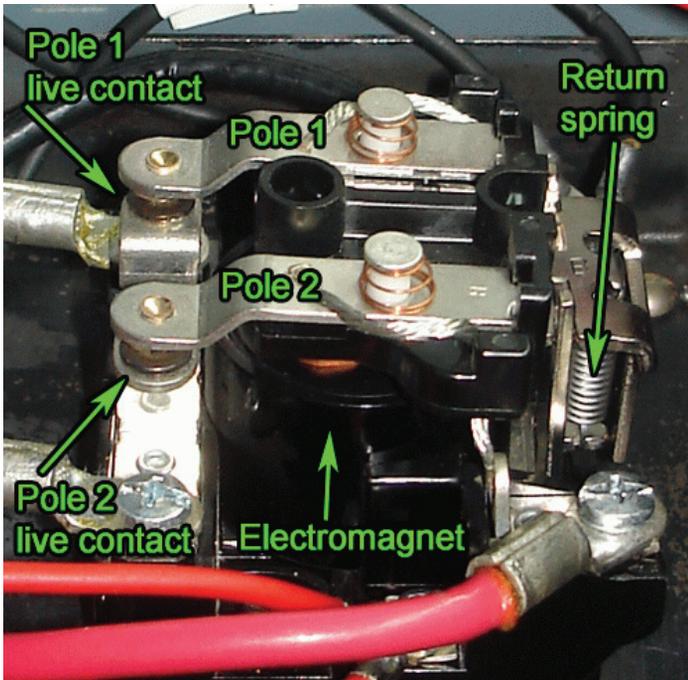


Figure 3: a double-pole, single-throw relay (DPST).

The next-most-complex relay type is the double-pole, single-throw (DPST) type. This relay has two separate center contacts, both of which are actuated by a single electromagnet (see figure 3). The center contacts (labeled “Pole 1” and “Pole 2” in the figure) are electrically isolated from each other. This type of relay is useful when you have two circuits that must each have its own independent connection to a source. (You could certainly achieve the same effect using two separate SPST relays, but the DPST relay would have fewer moving parts and, therefore, be slightly more reliable and easier to wire.)

We can continue building more complex relays by adding more poles. The DPDT (double-pole, double-throw) type would be an evolution of the DPST relay in figure 3. With such a relay, there would be an additional set of live contacts sitting above the two depicted that would be active when the electromagnet is off.

